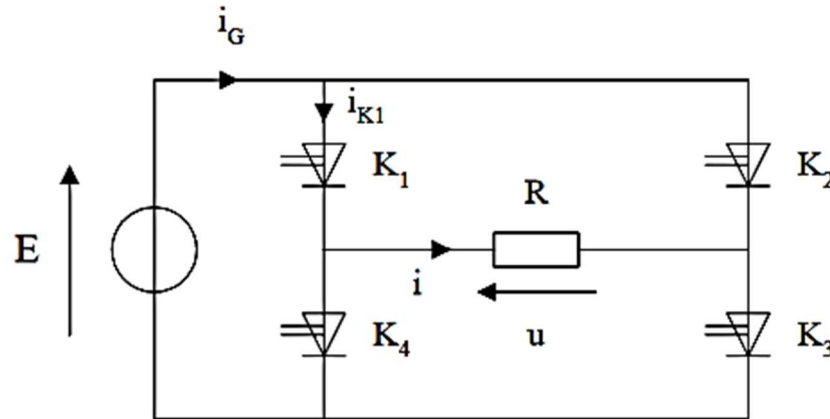


Series 4


Design methods of static converters at forced switching

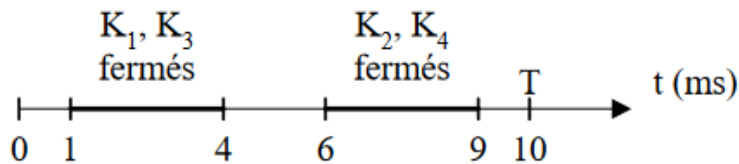Exercise 1

The following assembly is carried out using four electronic switches, operating in pairs.



The DC voltage generator has an e.m.f. E equal to 24 V. The load is a resistor with a value $R = 100 \Omega$. The operation of the switches is summarized in the diagram below:




The switches are supposed to be perfect.

- 1- Represent the chronograms: - the voltage u across the load terminals - currents i , i_{K1} and i_G .
- 2- Calculate the effective value of the voltage u . Deduce the effective value of the current i and the power received by the load.
- 3- Calculate the average value of the current delivered by the generator. Deduce the power supplied by the generator and the efficiency of the inverter. Comment ?

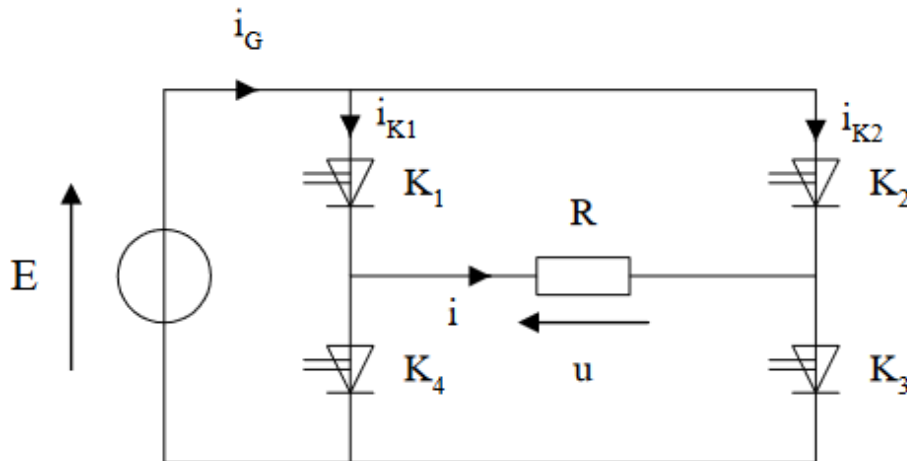Exercise 2

The next inverter is made up of four controlled electronic switches (K1 to K4) assumed to be perfect. E is a perfect direct voltage source with a value of 200 V. The load is a resistor with a value $R = 100 \Omega$.




The table below shows the conduction states of the switches.

	$0 < t < \alpha T/2$	$\alpha T/2 < t < T/2$	$T/2 < t < (1+\alpha)T/2$	$(1+\alpha)T/2 < t < T$
K ₁	Fermé	Fermé	Ouvert	Ouvert
K ₂	Ouvert	Fermé	Fermé	Ouvert
K ₃	Fermé	Ouvert	Ouvert	Fermé
K ₄	Ouvert	Ouvert	Fermé	Fermé

- 1- What type of conversion does a standalone inverter perform? Name an application of this type of converter.
- 2- Represent the voltage u across the load and the current i as a function of time circulating in it (we will take $\alpha = 1/3$).
- 3- Express the average value and the effective value of the current i as a function of E , R and α . Make the numerical application (with $\alpha = 1/3$).
- 4- Deduce the average value of the power supplied to the load.
- 5- Draw the chronograms of the currents i_{K1} , i_{K2} and i_G .
- 6- Express the average values of the currents i_{K1} , i_{K2} and i_G as a function of E , R and α . Make a digital application.
- 7- Deduce the average value of the power supplied by source E . Comment ?
- 8- What components can we use to make the switches?

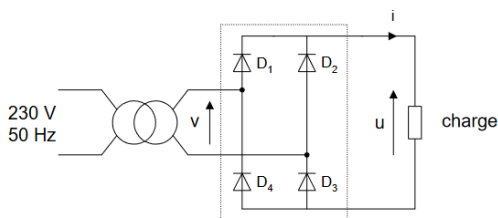Exercise 3

The rectifier assembly below is powered by the secondary of a transformer which provides a sinusoidal voltage v :



The diodes are assumed to be perfect (zero threshold voltage).

- 1-1- Calculate the period, the effective value and the maximum value of this voltage. Draw the chronogram $v(t)$. Data: the transformation ratio of the transformer is 0.21.
- 1-2- The load is a resistance $R_C = 17 \Omega$. Represent in time agreement the voltage across the load $u(t)$ and the voltage $v(t)$. Indicate the conduction intervals of the diodes.
- 1-3- Calculate the average value $\langle u \rangle$ of u . Draw the chronogram $i(t)$. Deduce the average value $\langle i \rangle$ of the current in the resistor.
- 1-4- Calculate the power consumed by the resistance.
- 2- The load of the bridge is now constituted by the armature of a direct current motor independent excitation, in series with a smoothing coil of negligible internal resistance and of sufficient inductance so that the armature current is considered constant: $I = 2.5 \text{ A}$.
- 2-1- We admit that the conduction intervals of the diodes are not modified. Deduce the form of the voltage u and its average value $\langle u \rangle$.
- 2-2- What is the relationship between the instantaneous values of the voltages u , u_L across the coil and u_m across the motor armature?
- 2-3- Justify that $\langle u_L \rangle = 0 \text{ V}$. Deduce the average value $\langle u_m \rangle$ of u_m .
- 2-4- The motor armature having a resistance $R = 1 \Omega$, calculate the value of its e.m.f. E .
- 2-5- Calculate the power consumed by the motor armature.