



Chapter 3

AC TO AC Converter

3.1 Single phase controller (phase control)

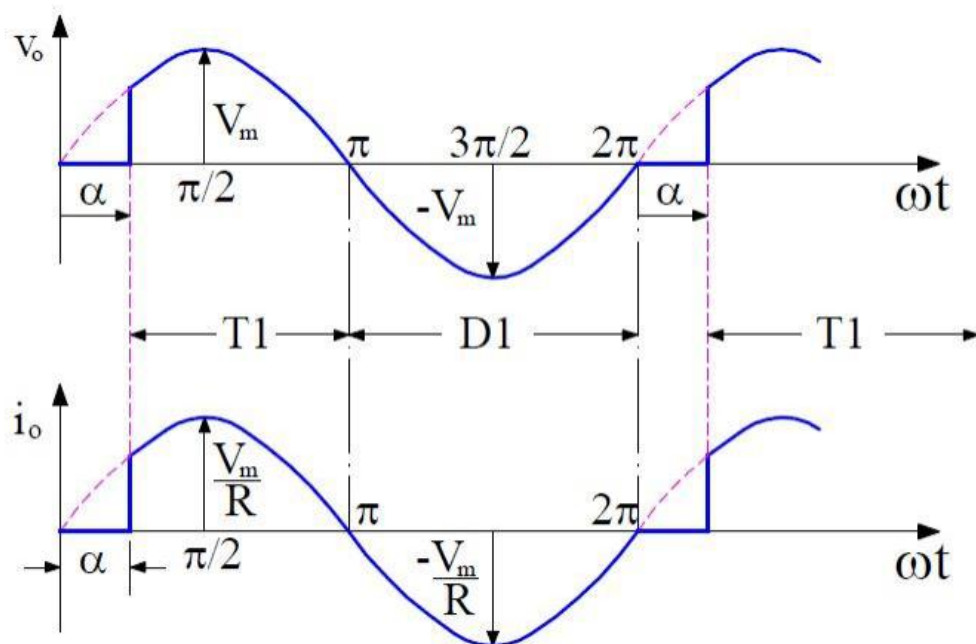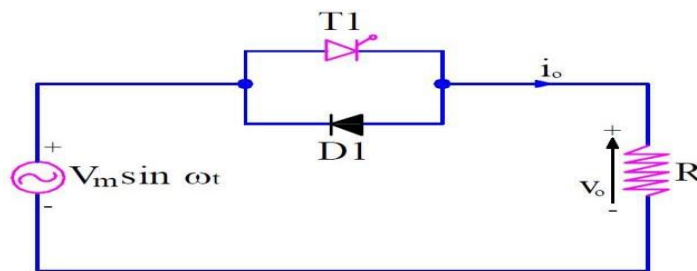3.1.1 Unidirectional controller

A single phase half wave AC voltage controller comprises of a thyristor connected in anti-parallel with a power diode. The circuit diagram is shown in figure below.



if input voltage, $v_s = V_m \sin \omega t = \sqrt{2} V_s \sin \omega t$
 delay angle of thyristor T_1 , $\omega t = \alpha$

the rms output voltage,

$$V_o = \left\{ \frac{1}{2\pi} \left[\int_{\alpha}^{\pi} 2V_s^2 \sin^2 \omega t \, d(\omega t) + \int_{\pi}^{2\pi} 2V_s^2 \sin^2 \omega t \, d(\omega t) \right] \right\}^{1/2}$$

$$= \left\{ \frac{2V_s^2}{4\pi} \left[\int_{\alpha}^{\pi} (1 - \cos 2\omega t) \, d(\omega t) + \int_{\pi}^{2\pi} (1 - \cos 2\omega t) \, d(\omega t) \right] \right\}^{1/2}$$

$$= V_s \left[\frac{1}{2\pi} \left(2\pi - \alpha + \frac{\sin 2\alpha}{2} \right) \right]^{1/2}$$

the average value of output voltage,

$$V_{dc} = \frac{1}{2\pi} \left[\int_{\alpha}^{\pi} \sqrt{2} V_s \sin \omega t \, d(\omega t) + \int_{\pi}^{2\pi} \sqrt{2} V_s \sin \omega t \, d(\omega t) \right]$$

$$= \frac{\sqrt{2} V_s}{2\pi} (\cos \alpha - 1)$$


$$\text{If, } \alpha = 0 \rightarrow \pi : V_o = V_s \rightarrow \frac{V_s}{\sqrt{2}}, \quad V_{dc} = 0 \rightarrow \frac{-\sqrt{2} V_s}{\pi}$$

EXAMPLE 1:-

A single-phase ac voltage controller in figure has a resistive load of $R=10\Omega$ and the input voltage is $V_s=120V$, 60Hz.

The delay angle of thyristor T_1 is $\alpha=\pi/2$. Determine,

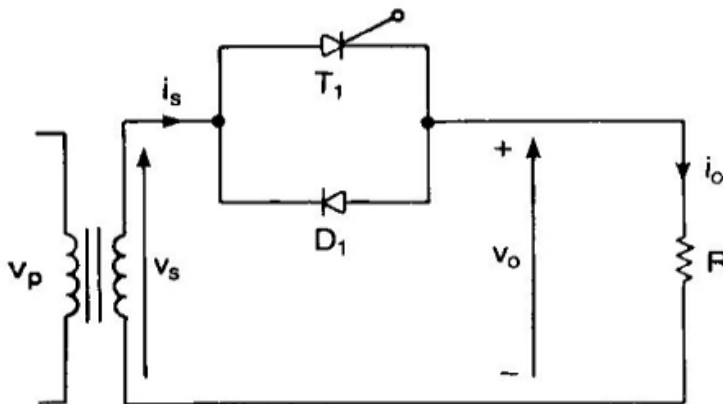- (a) The rms value of output voltage V_o**
- (b) The input power factor PF**
- (c) The average input current**



$$R = 10\Omega, V_s = 120\text{ V}, V_m = \sqrt{2} \times 120 = 169.7\text{ V}, \alpha = \frac{\pi}{2}$$

(a) the rms value of output voltage,

$$V_o = V_s \left[\frac{1}{2\pi} \left(2\pi - \alpha + \frac{\sin 2\alpha}{2} \right) \right]^{1/2} = 120 \sqrt{\frac{3}{4}} = 103.92\text{ V}$$

(b) the rms load current,

$$I_o = \frac{V_o}{R} = \frac{103.92}{10} = 10.392\text{ A}$$

$$\text{the load power, } P_o = I_o^2 R = 10.392^2 \times 10 = 1079.94\text{ W}$$

$$VA = V_s I_s = V_s I_o = 120 \times 10.392 = 1247.04\text{ VA}$$

the input power factor,

$$PF = \frac{P_o}{VA} = \frac{V_o}{V_s} = \left[\frac{1}{2\pi} \left(2\pi - \alpha + \frac{\sin 2\alpha}{2} \right) \right]^{1/2} = \sqrt{\frac{3}{4}} = \frac{1079.94}{1247.04} \\ = 0.866 \text{ (lagging)}$$

(c) the average output voltage,



$$V_{dc} = \frac{\sqrt{2} V_s}{2\pi} (\cos \alpha - 1) = -120 \times \frac{\sqrt{2}}{2\pi} = -27\text{ V}$$

the average input current

$$I_D = \frac{V_{dc}}{R} = -\frac{27}{10} = -2.7\text{ A}$$

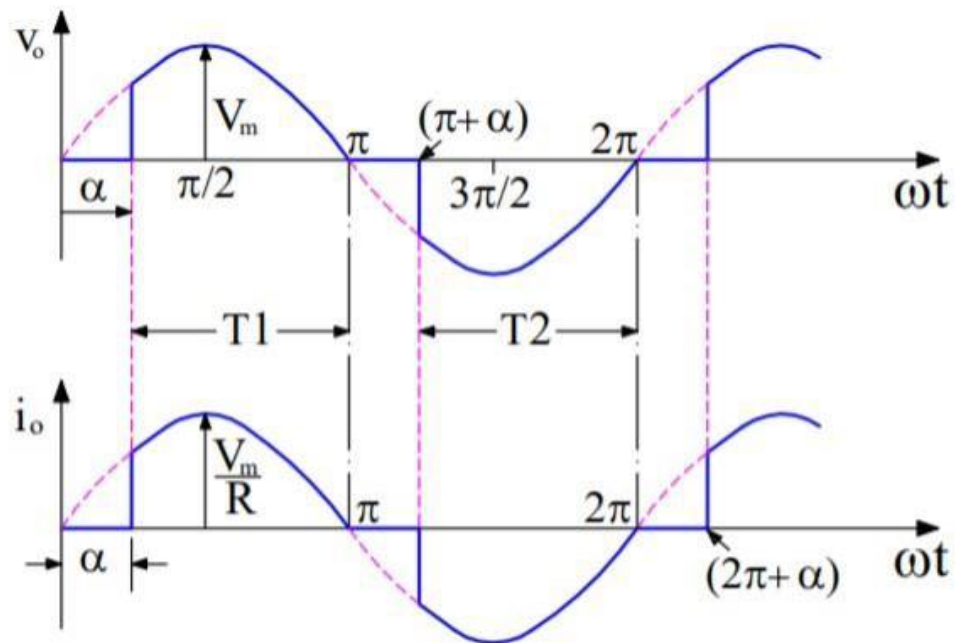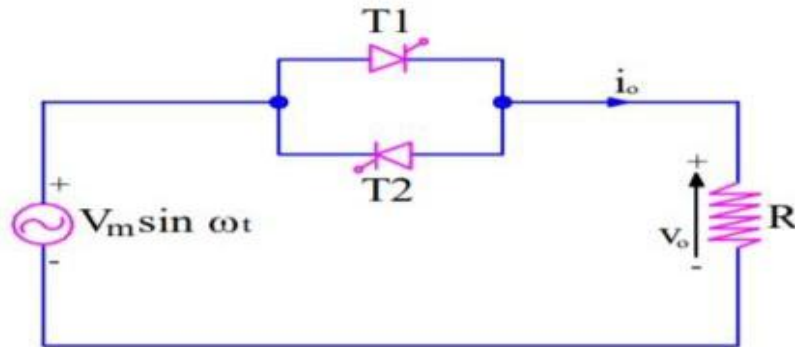3.2.2. Bidirectional controller

A single phase full wave AC voltage controller comprises of two thyristor connected in anti-parallel. The circuit diagram is shown in figure below.



if input voltage, $v_s = V_m \sin \omega t = \sqrt{2} V_s \sin \omega t$

delay angle of thyristor T_1 and T_2 , $\alpha_1 = \alpha_2 = \alpha$

the rms output voltage,

$$V_o = \left[\frac{2}{2\pi} \int_{\alpha}^{\pi} 2V_s^2 \sin^2 \omega t d(\omega t) \right]^{1/2} = \left[\frac{4V_s^2}{4\pi} \int_{\alpha}^{\pi} (1 - \cos 2\omega t) d(\omega t) \right]^{1/2}$$

$$= V_s \left[\frac{1}{\pi} \left(\pi - \alpha + \frac{\sin 2\alpha}{2} \right) \right]^{1/2}$$


If, $\alpha = 0 \rightarrow \pi : V_o = V_s \rightarrow 0$

EXAMPLE 2:-

A single-phase full-wave ac voltage controller in figure has a resistive load of $R=10\Omega$ and the input voltage is $V_s=120\text{V(rms)}$, 60Hz. The delay angle of thyristors T_1 and T_2 are equal :

$\alpha_1 = \alpha_2 = \pi/2$. Determine,

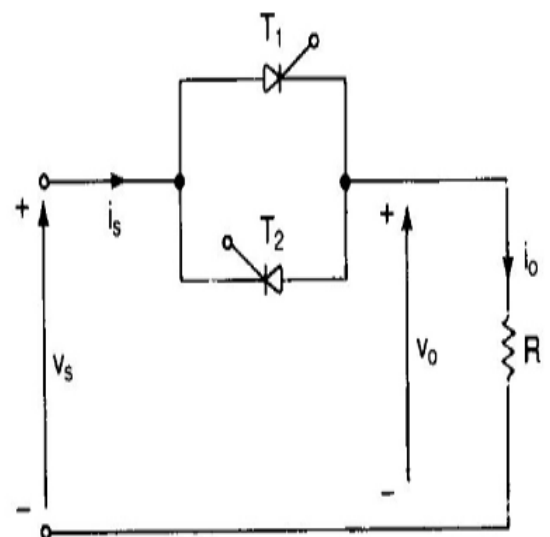- The rms output voltage V_o
- The input power factor PF
- The average current of thyristors I_A
- The RMS current of thyristors I_R



$$R = 10\Omega, V_s = 120\text{ V}, V_m = \sqrt{2} \times 120 = 169.7\text{ V}, \alpha = \frac{\pi}{2}$$

(a) the rms value of output voltage,

$$V_o = V_s \left[\frac{1}{\pi} \left(\pi - \alpha + \frac{\sin 2\alpha}{2} \right) \right]^{1/2} = \frac{120}{\sqrt{2}} = 84.85\text{ V}$$

(b) the rms load current,

$$I_o = \frac{V_o}{R} = \frac{84.85}{10} = 8.485\text{ A}$$

the load power, $P_o = I_o^2 R = 8.485^2 \times 10 = 719.95\text{ W}$

$$VA = V_s I_s = V_s I_o = 120 \times 8.485 = 1018.2\text{ W}$$

the input power factor,

$$PF = \frac{P_o}{VA} = \frac{V_o}{V_s} = \left[\frac{1}{\pi} \left(\pi - \alpha + \frac{\sin 2\alpha}{2} \right) \right]^{1/2} = \frac{1}{\sqrt{2}} = \frac{719.95}{1018.2} = 0.707 \text{ (lagging)}$$

(c) the average thyristor current,

$$I_A = \frac{1}{2\pi R} \int_{\alpha}^{\pi} \sqrt{2} V_s \sin \omega t \, d(\omega t) = \frac{\sqrt{2} V_s}{2\pi R} (\cos \alpha + 1) = \sqrt{2} \times \frac{120}{2\pi \times 10} = 2.7\text{ A}$$

(d) the rms value of the thyristor current,

$$I_R = \left[\frac{1}{2\pi R^2} \int_{\alpha}^{\pi} 2V_s^2 \sin^2 \omega t \, d(\omega t) \right]^{1/2} = \left[\frac{V_s}{4\pi R^2} \int_{\alpha}^{\pi} (1 - \cos 2\omega t) \, d(\omega t) \right]^{1/2} = \frac{V_s}{\sqrt{2} R} \left[\frac{1}{\pi} \left(\pi - \alpha + \frac{\sin 2\alpha}{2} \right) \right]^{1/2} = \frac{120}{2 \times 10} = 6\text{ A}$$