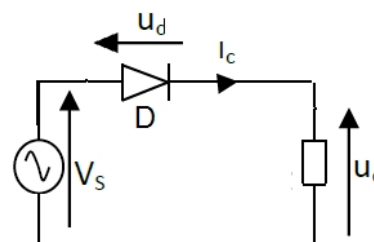


AC/DC Converters

Prob 01 :

A **single-phase half-wave rectifier** is supplied by a sinusoidal voltage source $V_s(\theta) = V_m \sin(\theta)$ with $V_m = 100$ V. The load is resistive $R = 10 \Omega$.

- a. Draw the waveforms of the input voltage $V_s(\theta)$, the output voltage $U_c(\theta)$ across the load, the current $I_c(\theta)$ through the load, and the voltage $U_d(\theta)$ across the diode D.



- b. Calculate the **average** and **rms** values of the load voltage.

Prob 02 :

If the load of «Prob 1» is replaced by an inductive load $Z = (10 + j10) \Omega$.


- a. Draw the waveforms of the input voltage $V_s(\theta)$, the output voltage $U_c(\theta)$ across the load, and the voltage $U_d(\theta)$ across the diode D.
- b. Calculate the **average** and **rms** values of the load voltage.
- c. A freewheeling diode is inserted in anti-parallel with the load,
 - Draw the waveforms of $U_c(\theta)$, and $U_d(\theta)$.
 - What is the **average** and **rms** values of the load voltage.

Prob 03 :

An a.c. supply of **230 V (rms)** is applied to a **half-wave rectifier** circuit through a transformer of turn ratio (**10 : 1**)

Assume the diode to be ideal, find :


- a. the **rms** value of the output d.c. voltage.
- b. the peak inverse voltage (PIV).

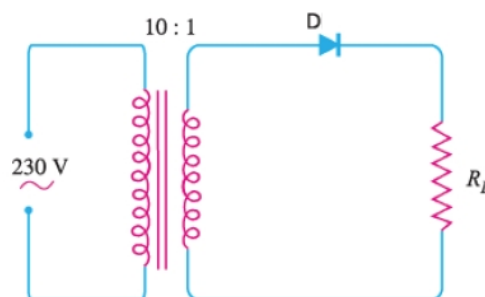

Prob 04 :

The single-phase rectifier shown in figure supplies a resistive load from a sinusoidal source $V_s = 220$ V / 50 Hz, $R = 5 \Omega$, $E = 180$ V.

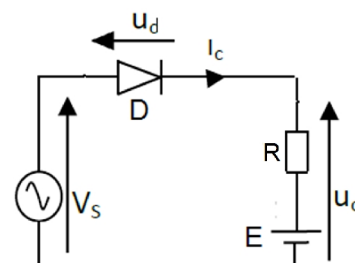
- a. Draw the waveforms of the input voltage $V_s(\theta)$, the output voltage $U_c(\theta)$ across the load, the current $I_c(\theta)$ through the load, and the voltage $U_d(\theta)$ across the diode D.



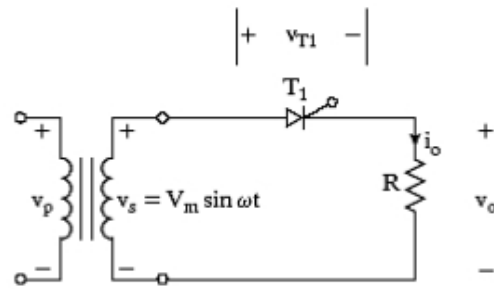- b. Calculate the **average** and **rms** values of the load voltage.

Prob 05:

Single-phase half-wave controlled rectifier is connected to **220 V, 50Hz** supply to feed **10Ω** resistor. If the firing angle $\alpha = 30^\circ$. Draw output voltage and voltage across the thyristor along with the supply voltage. Then, calculate,



- The **average** and **rms output voltage**
- The **average** and **rms output currents**
- Peak Inverse Voltage (PIV) of the thyristor.

Prob 06 :

Single-phase half wave converter is operated from a **120 V, 60-Hz** supply and the load resistive load is **R=10 Ω**. If the average output voltage is **25%** of the maximum possible average output voltage, calculate:

- The **delay angle**.
- The **average** and **rms output currents**.


Prob 07 :

Single phase half-wave-controlled rectifier is connected to **220 V, 50Hz** supply to feed **5 Ω** resistor in series with **10 mH** inductor if the firing angle $\alpha = 30^\circ$.

- Draw the waveform of load voltage if current extinction angle $\beta \approx (\pi + \text{impedance angle})$
- Find the **average** and **rms** value of output **voltage**.

Prob 08 :

Fig. (a) and Fig. (b) show the centre-tap and bridge type circuits having the same loadresistance and transformer turn ratio. The primary of each is connected to 230V, 50 Hz supply. Assume the diodes to be ideal:

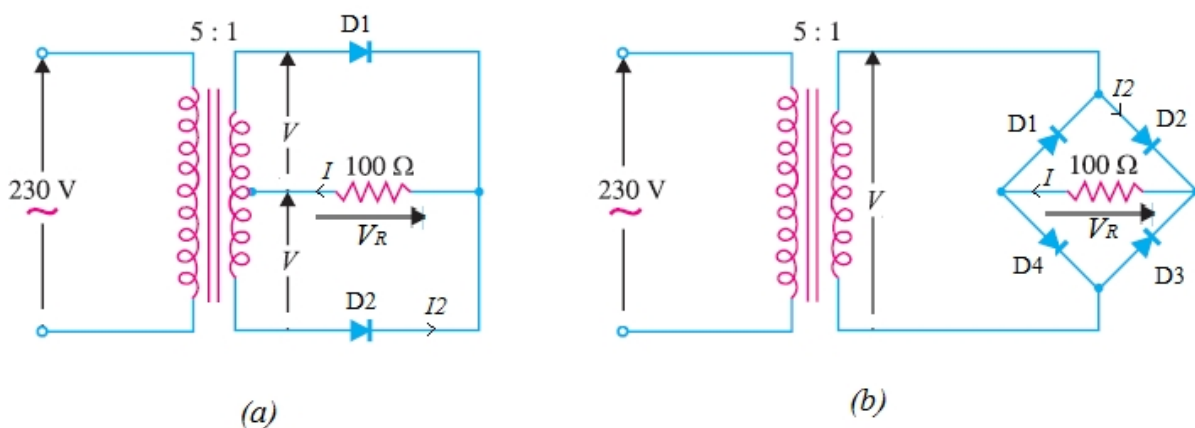

- Draw the waveforms of $V_R(\theta)$, $I_2(\theta)$ in each case
- Find the **average** output voltage in each case.
- Peak Inverse Voltage (**PIV**) of diodes for each case.

Prob 09 :


Single – phase **center tap** controlled rectifier has load of $R = 15 \Omega$ and, $V_s = 220 \sin 314t$ and **unity transformer ratio**. If it is required to obtain an average output voltage of **70 %** of the maximum possible average output voltage, calculate:

- The **delay angle**.
- The **average** and **rms output currents**.
- The **peak inverse voltage (PIV)**.

Prob 10 :

The full-wave controlled **bridge rectifier** has an AC input of **120 V** at **50 Hz** and a **20 Ω** load resistor. The delay angle is **40°**.


- Draw the load voltage and current (V_C, i_c), thyristor and diode currents ($i_{T1}, i_{T2}, i_{D1}, i_{D2}$), and supply current (i).
- Calculate the average and rms current in the load.

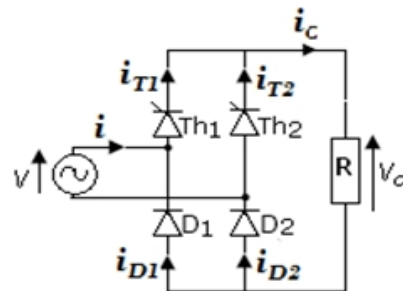

Prob11 :

Power is supplied to a load resistor $R=10 \Omega$ from a three-phase supply of balanced sinusoidal voltages using half-wave bridge circuit of figure below. The three diodes may be considered as ideal switches. Draw:

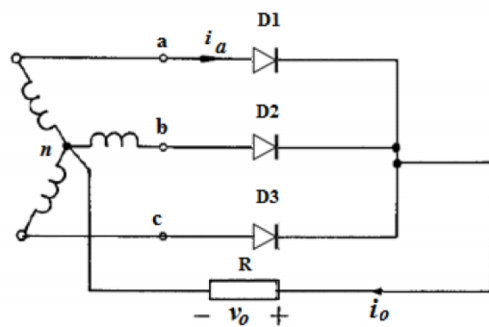- the output current waveform $i_o(\omega t)$ with respect to the phase voltage $V_{an}(\omega t) = V_m \sin \omega t$.
- the phase current waveform $i_a(\omega t)$ in phase-a with respect to the phase voltage $V_{an}(\omega t) = V_m \sin \omega t$.
- Show that the rms value of the phase current is: $i_{a_{rms}} = 0.485.(V_m/R)$




Hence, calculate $I_{a_{rms}}$ of the phase current.

Prob 12 :

Power is supplied to a load resistor R from a three-phase supply of balanced sinusoidal voltages using full-wave uncontrolled bridge circuit of figure below. The six diodes may be considered as ideal switches.

If the supply voltage for phase-a is $v_{an}(\omega t) = V_m \sin (\omega t)$, and the ligne-to-line voltage is $v_{ab}(\omega t) = \sqrt{3} V_m \sin \left(\omega t + \frac{\pi}{6} \right)$

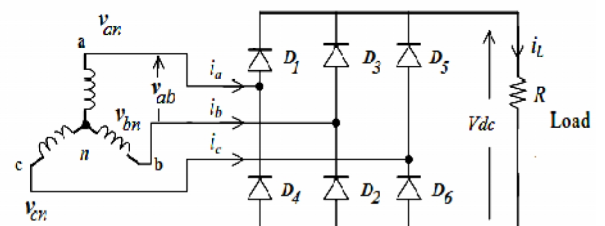
- Calculate $\langle V_{dc} \rangle$ and $\langle i_L \rangle$ if $V_m=300 \text{ V}$, $R=50 \Omega$



AC/AC Converters

Prob13 :

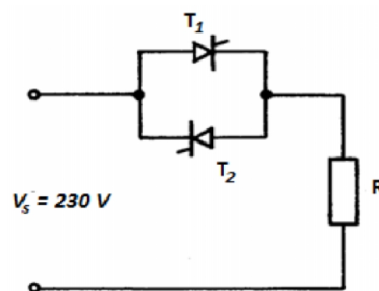A single-phase full-wave a.c. voltage controller consists of two thyristors connected in inverse-parallel as shown in figure. The supply voltage is $V_s = 230 \text{ V}$ (rms) at 50 Hz. The controller is used as a light dimmer to control the light intensity of a group of lamps with total resistance of 10Ω . The triggering mode of the thyristors is symmetrical with $\alpha = 60^\circ$.



- Sketch compatible waveforms for the load and thyristor voltages.
- Sketch compatible waveforms for the load and thyristor current.
- Calculate the rms value of the load voltage.
- Calculate the rms value of the load current.

Prob 14 :

If thyristor T2 of «Prob 13» is replaced by a diode,

- what will be the compatible waveforms for the load and diode voltages.
- Calculate the rms value of the load voltage.

Prob15 :

A single-phase full-wave AC voltage controller supplies an RL load. The supply rms voltage is 120 V, 60 Hz. The load has $R=2.5 \Omega$ and $L=6.5 \text{ mH}$, the firing delay angles of thyristors are equal: $\alpha_1 = \alpha_2 = \pi/2$. If the extinction angle (β) is 220° :

- Sketch the waveforms for the load and thyristor voltages.
- Calculate the rms value of the load voltage.

Prob16 :


Rework the same «Problem 15» assuming that the firing delay angles of the thyristors are equal to: $\alpha_1 = \alpha_2 = \pi/6$.

DC/DC Converters

Prob17 :

A transistor dc chopper circuit (Buck converter) is supplied with power from an ideal battery of 100 V. The load voltage waveform consists of rectangular pulses of duration 1 ms in an overall cycle time of 2.5 ms. Calculate, for resistive load of 10Ω .

- The duty cycle D.
- The average value of the output voltage $\langle V_0 \rangle$.
- The rms value of the output voltage $V_{0\text{rms}}$.

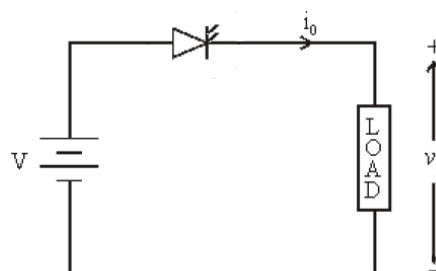

Prob18 :

A Chopper circuit is operating at a frequency of 2 kHz on a 460 V supply. If the average value of the load voltage is 350 volts,


- Calculate the conduction duration of the switch in each cycle.
- Sketch the waveforms for the load and switch voltages.

DC/AC Converters

Prob19 :

The single-phase half-bridge inverter shown in figure has a resistive load of $R = 100 \Omega$ and the d.c. input voltage $E = 200 \text{ V}$. If the inverter output voltage is a square wave:


- Sketch the output voltage waveform
- Determine the rms value of the output voltage
- Sketch one switch current and give its average value.
- What is the peak inverse voltage of the switches?

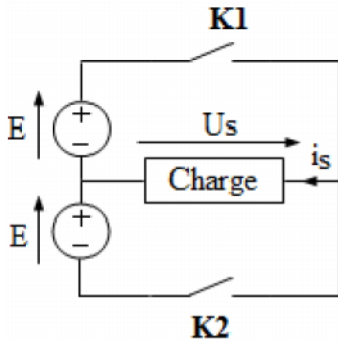

Prob20 :


In the inverter of problem 18, the control logic for power electronics devices is so adjusted (see diagram below) that the output voltage waveform produced is a quasi-square.

- Draw the output voltage and load current waveforms for $\alpha=1/3$ and output voltage frequency $f_r=50 \text{ Hz}$.
- Determine the value of the rms output voltage in terms of E and α . Calculate rms output voltage for $\alpha=1/3$.

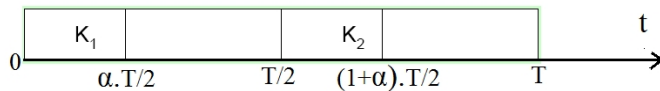

Prob21 :

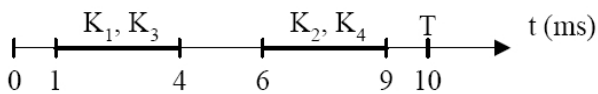A single-phase bridge inverter has a resistive load of 100Ω and input voltage of 24 V . The operation of the switches is summarized in the diagram below:



- Draw the output voltage u and load current waveforms i .
- Draw current waveforms i_{k1} and i_G .
- Calculate the rms output voltage.

