



PW AVANCED POWER ELECTRONIC

PW N°5

Static reactive power compensators

Objective :

The primary objectives of static reactive power compensators, such as Static VAR Compensators (SVCs), include:

1. **Voltage regulation:** They help maintain stable voltage levels in power systems by compensating for reactive power imbalances. This is crucial for preventing voltage fluctuations and ensuring consistent power supply quality.
2. **Power factor correction :** SVCs adjust the power factor by controlling reactive power, which improves system efficiency and reduces energy losses. A better power factor means more efficient use of active power.
3. **System stability enhancement :** By providing or absorbing reactive power, SVCs enhance system stability, reduce power losses, and prevent over-voltages. This helps in maintaining grid stability during load variations.
4. **Load balancing:** SVCs can balance three-phase loads, reducing equipment overload and additional losses associated with asymmetric loads.
5. **Improvement of power quality :** They mitigate issues like voltage sags and flicker, ensuring smoother operation of electrical systems.

Handing:


- 1- Study of the different types of compensation and compare them with respect to the stability of the voltage at the terminals of the load impedance.
- 2- Study of the reduction of power losses.
- 3- Improvement of the power factor $\cos \phi$.

Parallel compensation:

1 Assembly: Carry out the following assembly, taking a resistive-inductive load:



PW AVANCED POWER ELECTRONIC

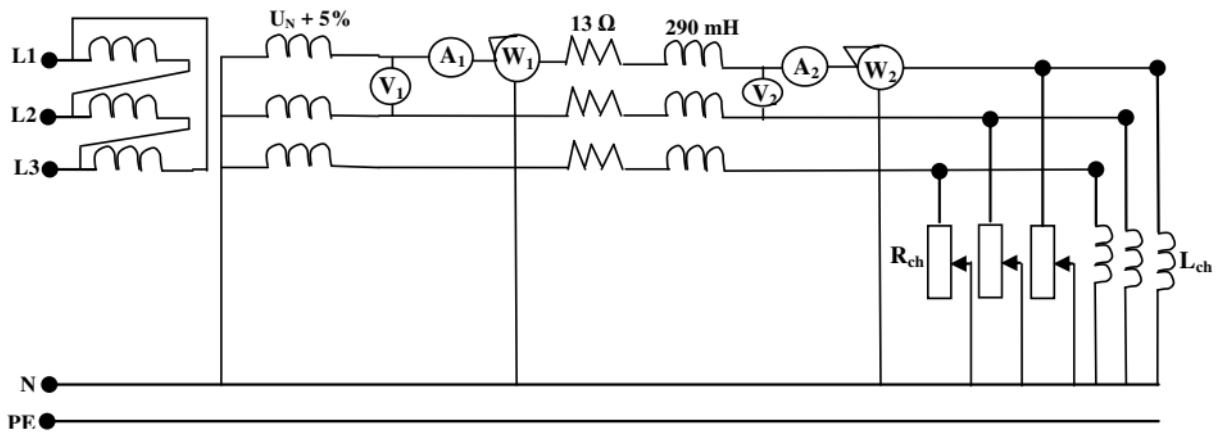

Operating mode


1. In order to demonstrate the main role of this type of compensation, it is sufficient to study the line without operating capacities.
2. Set the inductive load to $L_{ch} = 2.4 \text{ H}$
3. Vary the resistive load by 100%, 80%, 60% and 40%
4. Measure the parameters: voltage U_1 , current I_1 , active power P_1 and reactive power Q_1 at the beginning of the line as well as voltage U_2 , current I_2 , active power P_2 and reactive power Q_2 and $\cos \varphi_2$ at the end of the line;
5. Change the value of the load inductance to $L_{ch} = 1.2 \text{ H}$ and repeat the same measurements
6. Transfer the measurements to the table below:



PW AVANCED POWER ELECTRONIC

L_{ch} (H)	R_{ch} (%)	U_1 (V)	I_1 (A)	P_1 (W)	Q_1 (VAR)	U_2 (V)	I_2 (A)	P_2 (W)	Q_2 (VAR)	$\cos\phi_2$	$\Delta P = P_1 - P_2$	$\Delta Q = Q_1 - Q_2$
2,4	100											
	80											
	60											
	40											
1,2	100											
	80											
	60											
	40											

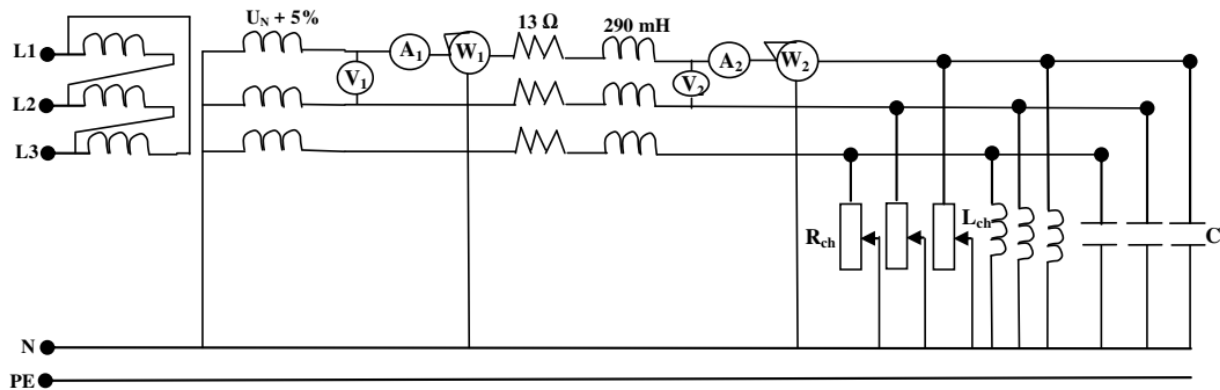7. Connect the compensation capacitors in parallel



8. For $L_{ch} = 2.4$ H take $C = 4\mu F$ and for $L_{ch} = 1.2$ H take $C = 8\mu F$; enter the measurements in the table below:



PW AVANCED POWER ELECTRONIC

C(μ F)	L _{ch} (H)	R _{ch} (%)	U ₁ (V)	I ₁ (A)	P ₁ (W)	Q ₁ VAR	U ₂ (V)	I ₂ (A)	P ₂ (W)	Q ₂ VAR	cos ϕ_2	$\Delta P =$ P ₁ -P ₂	$\Delta Q =$ Q ₁ -Q ₂	
4	2,4	100												
		80												
		60												
		40												
8	1,2	100												
		80												
		60												
		40												

9. Compare the results of the load voltage measurements U₂ before and after compensation for the same load?
10. What do you notice about the value of the load factor cos ϕ_2 ?
11. How do the active and reactive power losses vary before and after compensation for the same load?